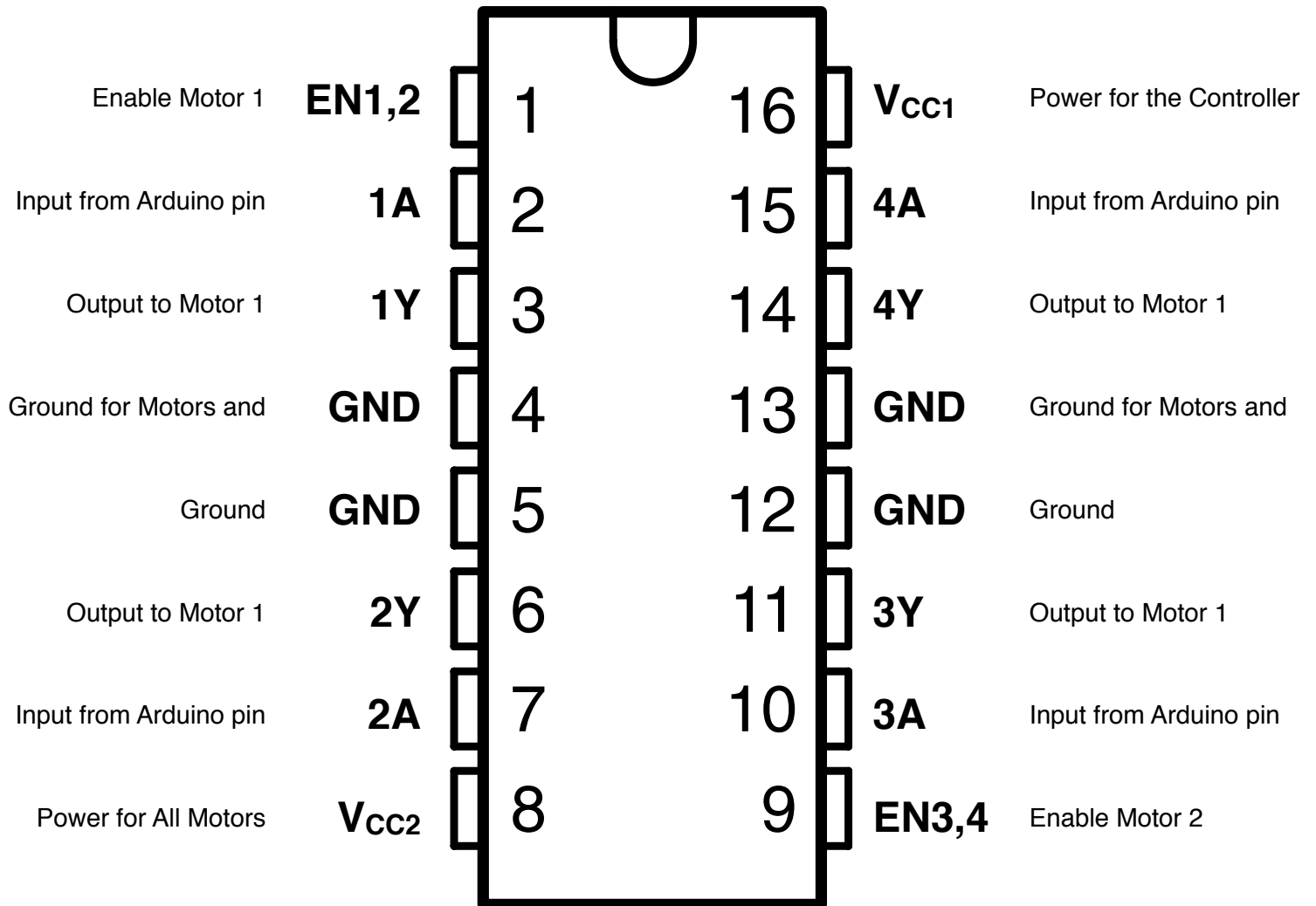


L293D, a Motor Controller


(called a Quad Half-H Bridge, suitable for two motors)

Motor 1

Motor 2




HIGH → LOW

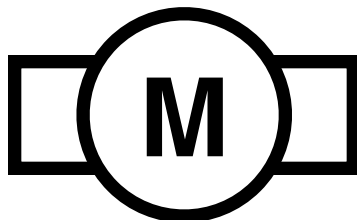


Motor spins

LOW ← HIGH

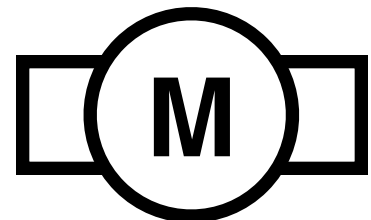

Motor spins

Breadboard View

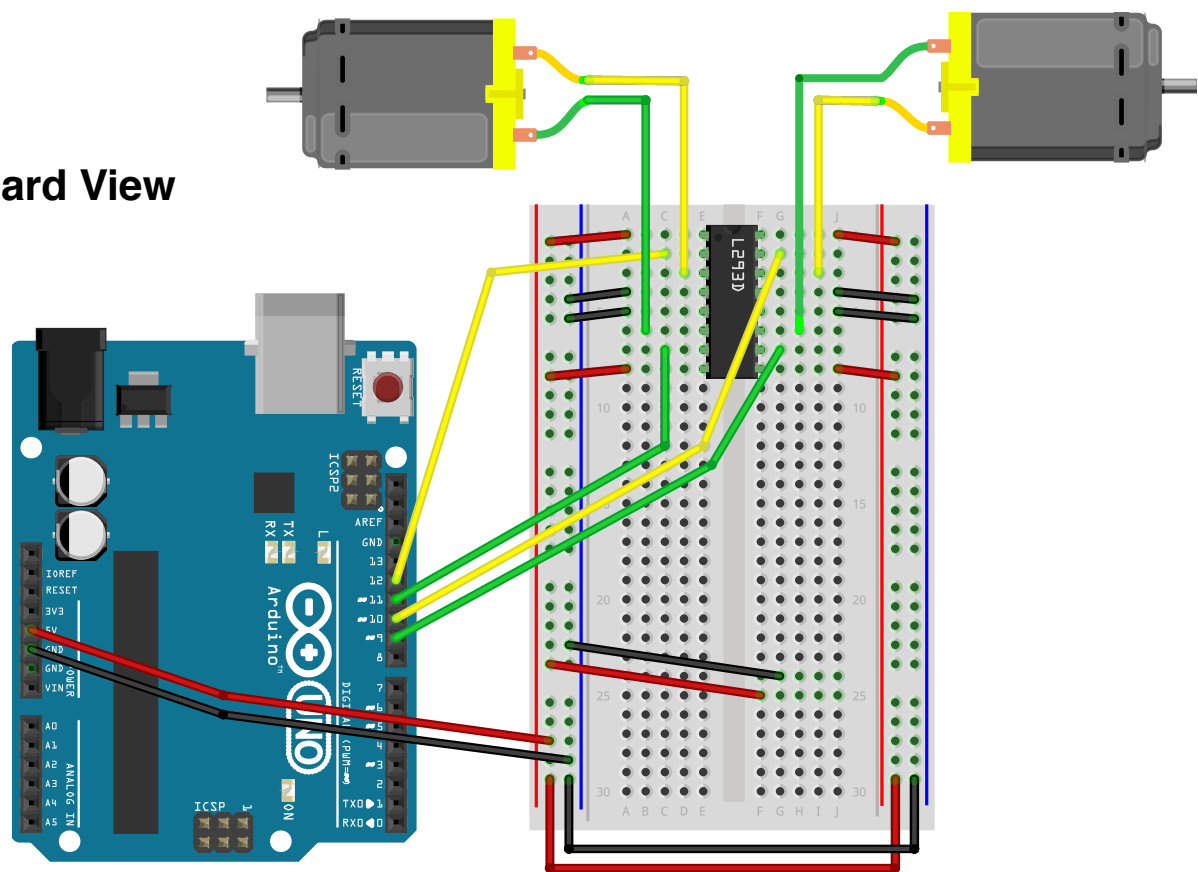

Schematic View

